

Interlink Electronics FSR™ Force Sensing Resistors™

FSR™ Integration Guide

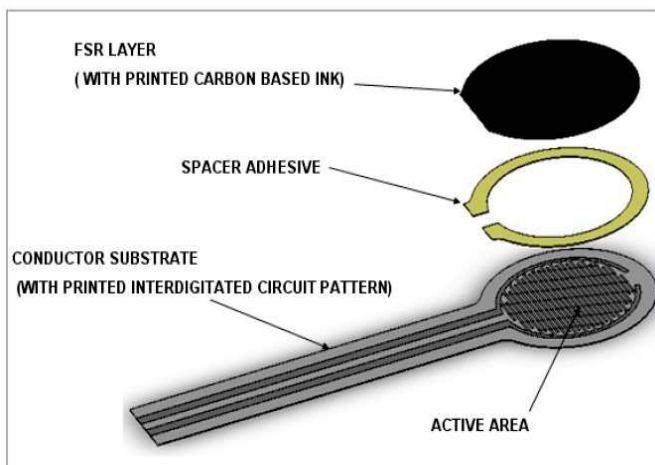


Figure 1: Basic FSR Construction


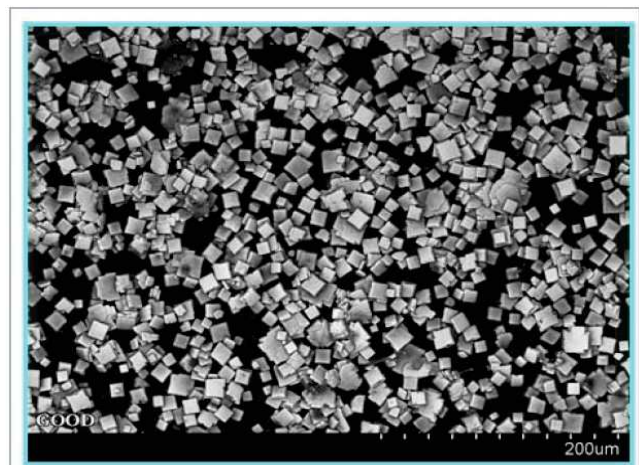
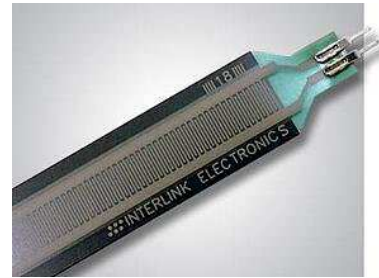
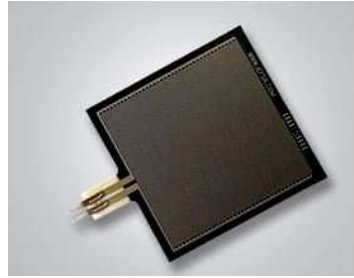
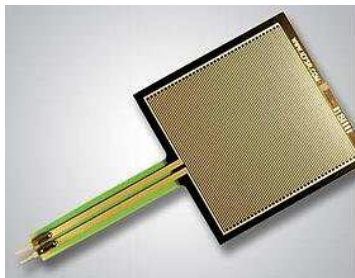
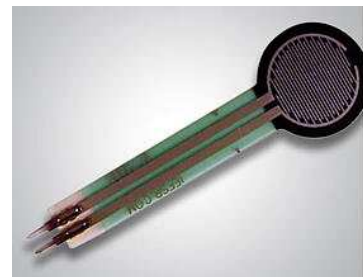


Figure 2: FSR Ink Micrograph

FSR 400 series


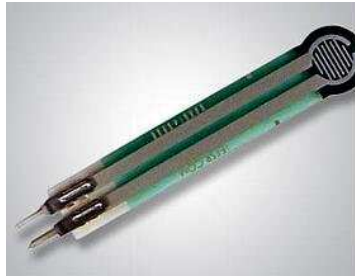


FSR 402 Data Sheet

FSR 400 Series Round Force Sensing Resistor



| m [g] | F [N] | RF [Ω] |
|-------|-------|-----------------|
| 50 | 0,5 | 100000 |
| 100 | 1 | 20000 |
| 200 | 2 | 7000 |
| 500 | 5 | 1700 |
| 1000 | 10 | 900 |
| 5000 | 50 | 280 |

Figure 1 - Force Curve

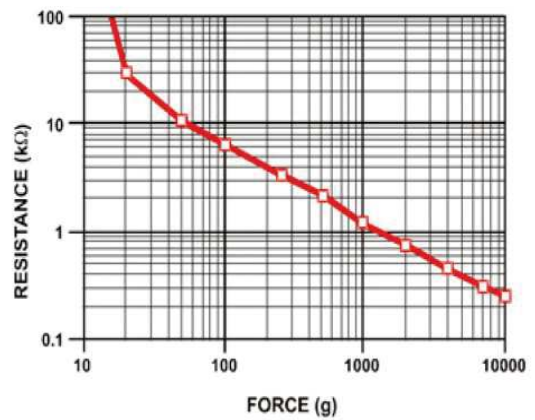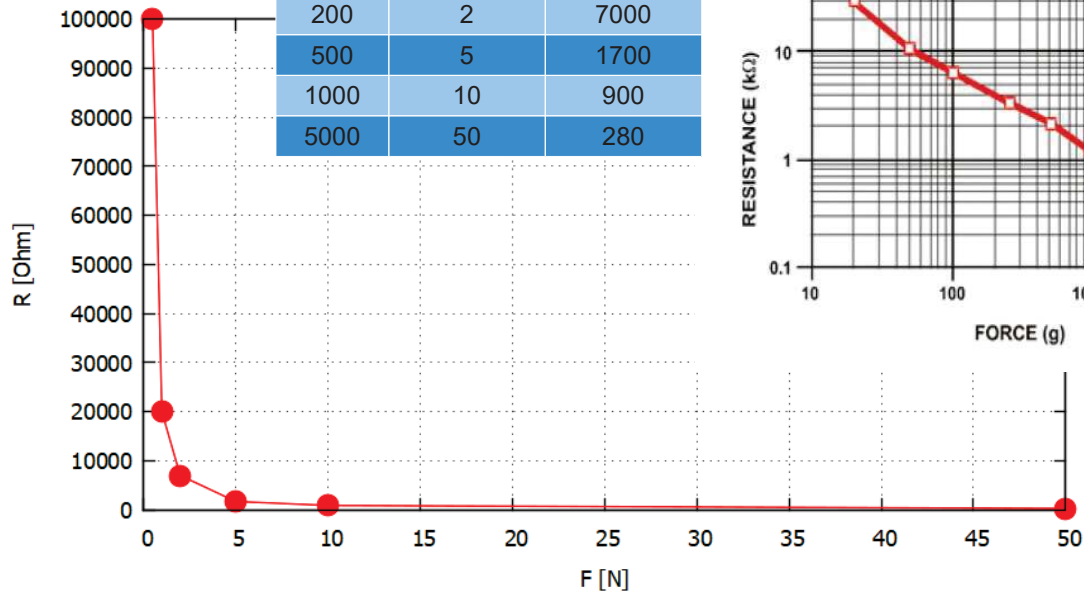

Meranie odporu

Ako zmerať A/D prevodníkom hodnotu odporu?

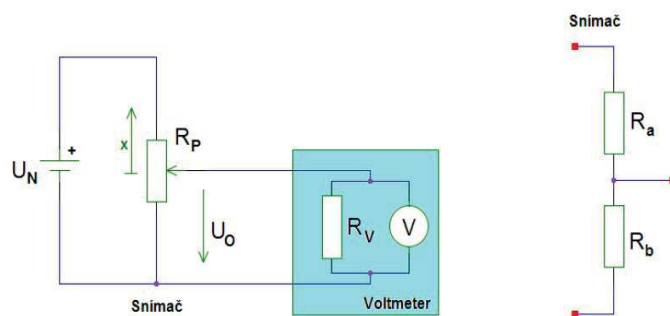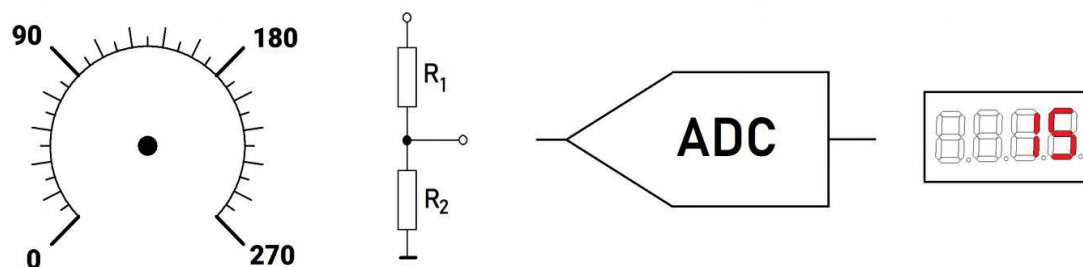


Obr. 2. Schéma zapojenia.

6.0 Measurement Techniques


6.1 Circuit

Voltage Divider


Figure 9: FSR Voltage Divider


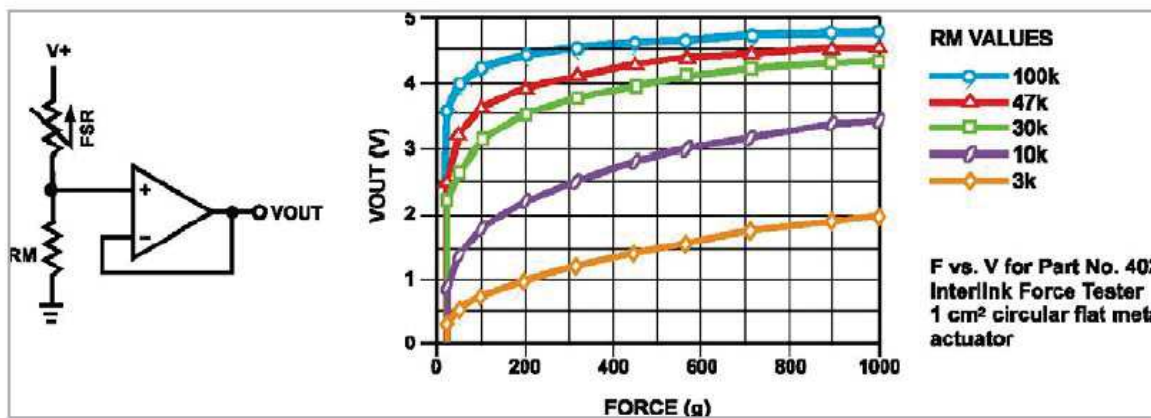


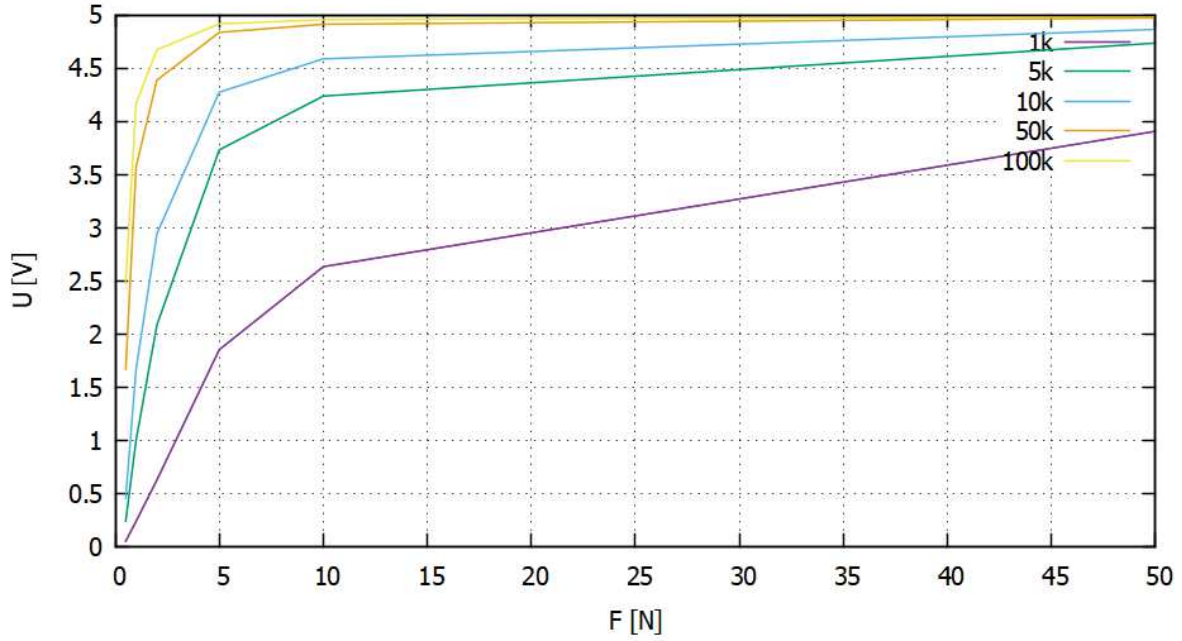Vstupna charakteristika delica (senzor HORE)



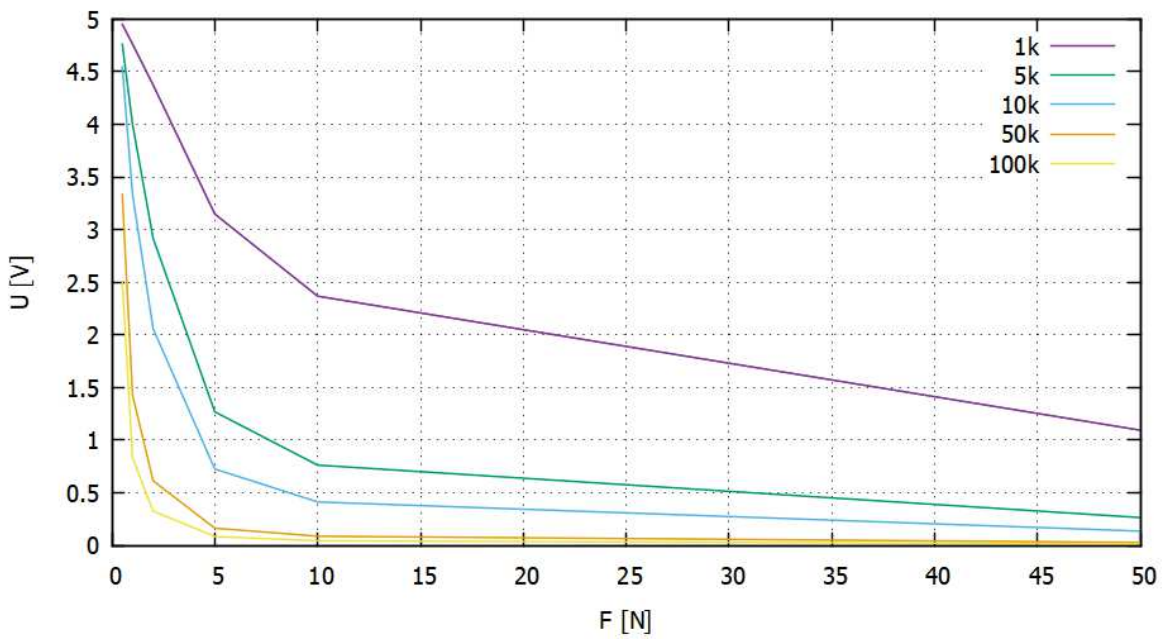Vstupna charakteristika delica (senzor dolu)



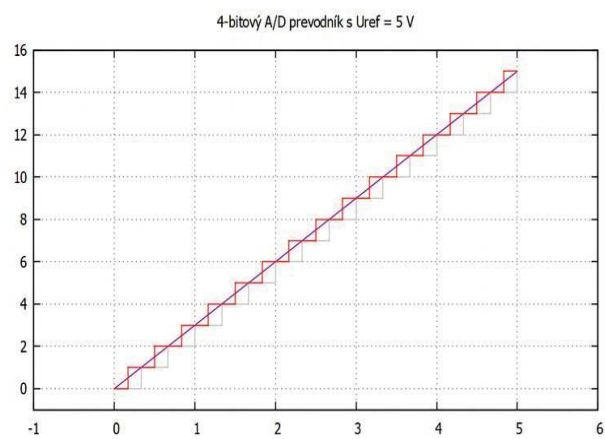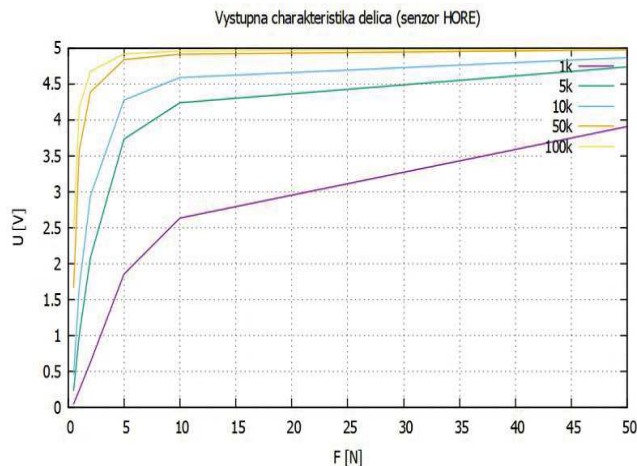

Výsledok merania 4-bitovým prevodníkom by vyzeral takto:

| | | | | | | | | |
|-----------|---|----|----|----|----|-----|----|----|
| Force [N] | 0 | 1 | 2 | 3 | 4 | ... | 49 | 50 |
| ADC [-] | 0 | 10 | 13 | 15 | 15 | ... | 15 | 15 |

Pre 10-bitový prevodník to nebude oveľa lepšie!

FSR Current-to-Voltage Converter

In this circuit, the FSR device is the input of a current-to-voltage converter. The output of this amplifier is described by the equation:

$$V_{OUT} = V_{REF} \cdot \left(-\frac{R_G}{R_{FSR}} \right)$$



With a positive reference voltage, the output of the op-amp must be able to swing below ground, from 0V to -VREF, therefore dual sided supplies are necessary. A negative reference voltage will yield a positive output swing, from 0V to +VREF.

$$V_{out} = \frac{-V_{ref} \cdot R_G}{R_{FSR}}$$

$$V_{OUT} = \frac{(-R_G \cdot V_{REF})}{R_{FSR}}$$

VOUT is inversely proportional to RFSR. Changing RG and/or VREF changes the response slope. The following is an example of the sequence used for choosing the component values and output swing:

Figure 15: FSR Current-to-Voltage

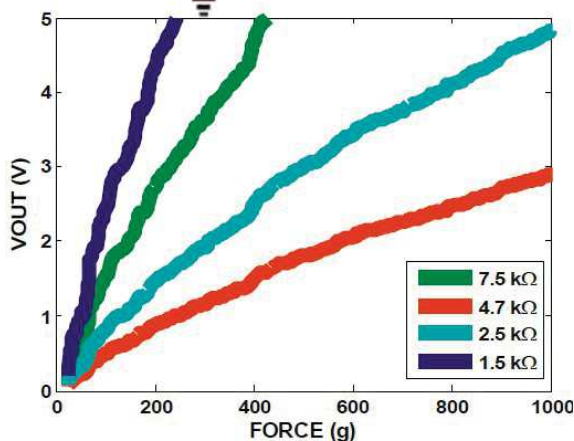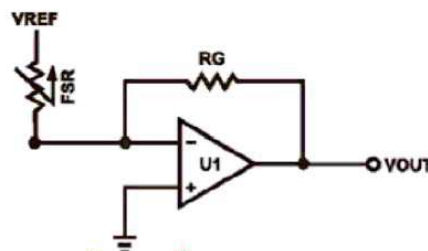

Výpočet I.

Čo vieme:


$$R_{FSR} = 250\Omega \dots 1M\Omega$$

$$V_{out} = \frac{-V_{ref} * R_G}{R_{FSR}}$$

Zvolíme si pre jednoduchosť, že
 $V_{Ref} = -1$ [V] (znamienko je dôležité)

Výpočet II.

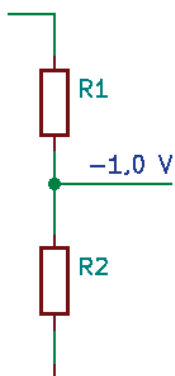Zvolíme si pre jednoduchosť, že
 $V_{Ref} = -1$ [V] (znamienko je dôležité)



<https://damien.douxchamps.net/elec/resdiv/>

Podobný kompletný výpočet a meranie tiež tu:


<https://www.youtube.com/watch?v=VtxFtzWlTgg>

Vylepšenie na záver

Analog Engineer's Circuit Amplifiers
Low-Pass, Filtered, Inverting Amp



AC Simulation Results

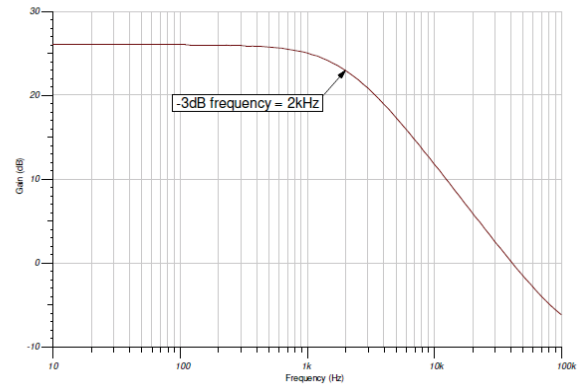

Design Goals

| Input | | Output | |
|------------|------------|------------|------------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} |
| -0.1V | 0.1V | -2V | 2V |

Design Description

This tunable low-pass inverting amplifier circuit amplifies the signal and provides a tunable cutoff frequency for this circuit. The frequency response of this circuit is the same as that of a passive RC filter, except that the output is amplified by the pass-band gain of the amplifier. Low-pass filters are often used in audio signal chains and are sometimes called bass-boost filters.

